

---

# **Computer Architecture**

## **Chapter 3-1**

### **Arithmetic for computers**



# Detecting Overflow

---

- **No overflow when adding a positive and a negative number**
- **No overflow when signs are the same for subtraction**
- **Overflow occurs when the value affects the sign:**
  - overflow when adding two positives yields a negative
  - or, adding two negatives gives a positive
  - or, subtract a negative from a positive and get a negative
  - or, subtract a positive from a negative and get a positive
- **Consider the operations  $A + B$ , and  $A - B$** 
  - Can overflow occur if  $B$  is 0 ?
  - Can overflow occur if  $A$  is 0 ?

# Effects of Overflow

---

- **An exception (interrupt) occurs**
  - Save PC in exception program counter (EPC) register
    - `mfc0` (move from coprocessor reg) instruction can retrieve EPC value, to return after corrective action
  - Control jumps to predefined address for exception
- **Details based on software system / language**
  - example: flight control vs. homework assignment
- **Don't always want to detect overflow**
  - Overflow MIPS instructions: `add`, `addi`, `sub`
  - No overflow MIPS instructions: `addu`, `addiu`, `subu`

*note: `addiu` still sign-extends! (negative constant)*

*note: `sltu`, `sltiu` for unsigned comparisons*


# Arithmetic for Multimedia

---

- **Graphics and media processing operates on vectors of 8-bit and 16-bit data**
  - Use 64-bit adder, with partitioned carry chain
    - Operate on  $8 \times 8$ -bit,  $4 \times 16$ -bit, or  $2 \times 32$ -bit vectors
  - SIMD (single-instruction, multiple-data)
- **Saturating operations**
  - On overflow, result is largest representable value
    - c.f. 2s-complement modulo arithmetic
  - E.g., clipping in audio, saturation in video


# Half Adder (1-bit)

---

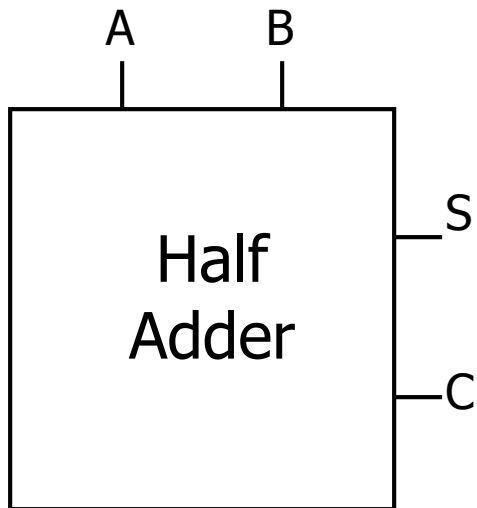

A	B	S(um)	C(arry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Half Adder (1-bit)

 


A	B	S(um)	C(arry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB$$

# Full Adder

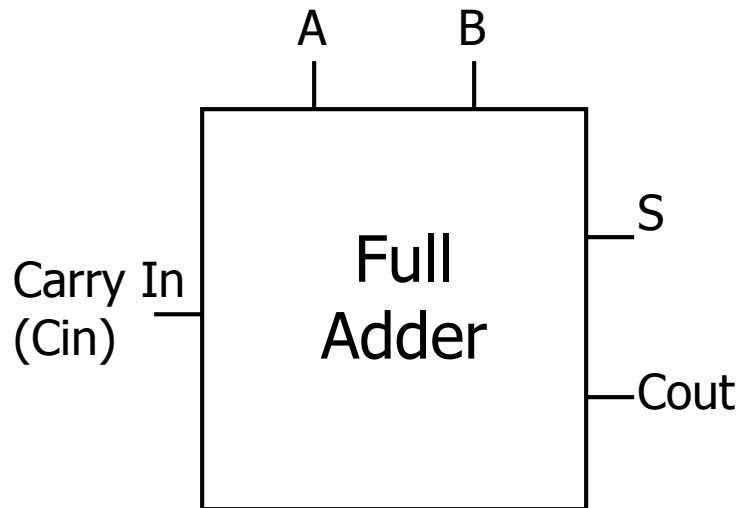

Cin	A	B	S(um)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Full Adder

		AB			
	<b>Cin</b>	00	01	11	10
0		0	1	0	1
1		1	0	1	0

$$\begin{aligned}
 S &= \overline{\text{Cin}}\overline{A}B + \overline{\text{Cin}}A\overline{B} + \text{Cin}A\overline{B} + \overline{\text{Cin}}A\overline{B} \\
 &= \text{Cin}(\overline{A}B + A\overline{B}) + \overline{\text{Cin}}(\overline{A}B + A\overline{B}) \\
 &= \text{Cin}(A \oplus B) + \overline{\text{Cin}}(A \oplus B) \\
 &= \text{Cin} \oplus A \oplus B
 \end{aligned}$$

Cin	A	B	S(um)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		AB			
	<b>Cin</b>	00	01	11	10
0		0	0	1	0
1		0	1	1	1

$$\text{Cout} = \text{Cin}B + \text{Cin}A + AB$$

Or


		AB			
	<b>Cin</b>	00	01	11	10
0		0	0	1	0
1		0	1	1	1

$$\text{Cout} = AB + \text{Cin}(\overline{A}B + A\overline{B}) = AB + \text{Cin}(A \oplus B)$$

# Full Adder

$$S = C_{in} \oplus A \oplus B$$


$$C_{out} = AB + C_{in}(A \oplus B)$$

 


# Full Adder

$$S = C_{in} \oplus A \oplus B$$


$$C_{out} = AB + C_{in}(A \oplus B)$$

 

# 4-bit Ripple Adder using Full Adder

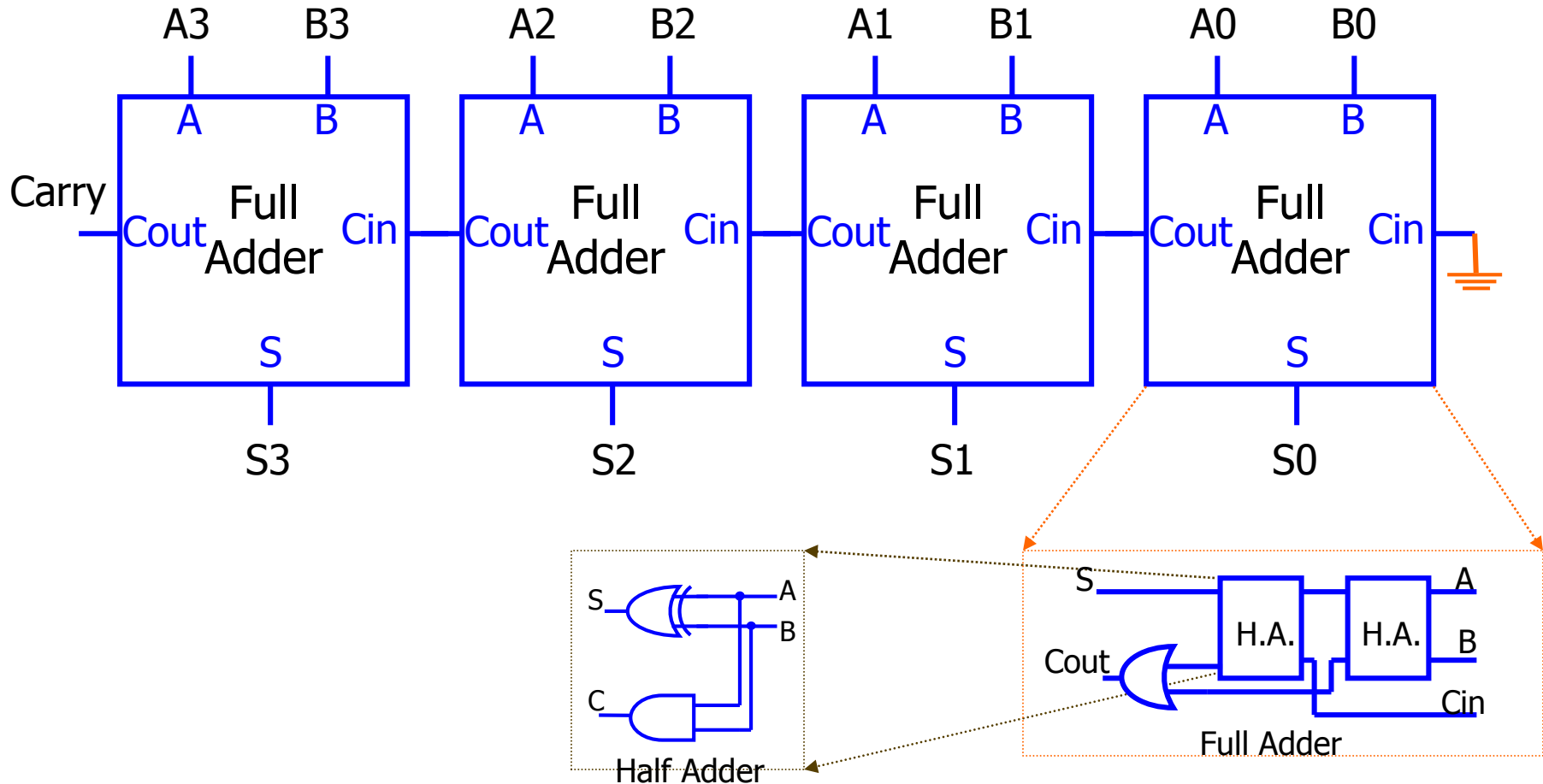

# Subtractor Design

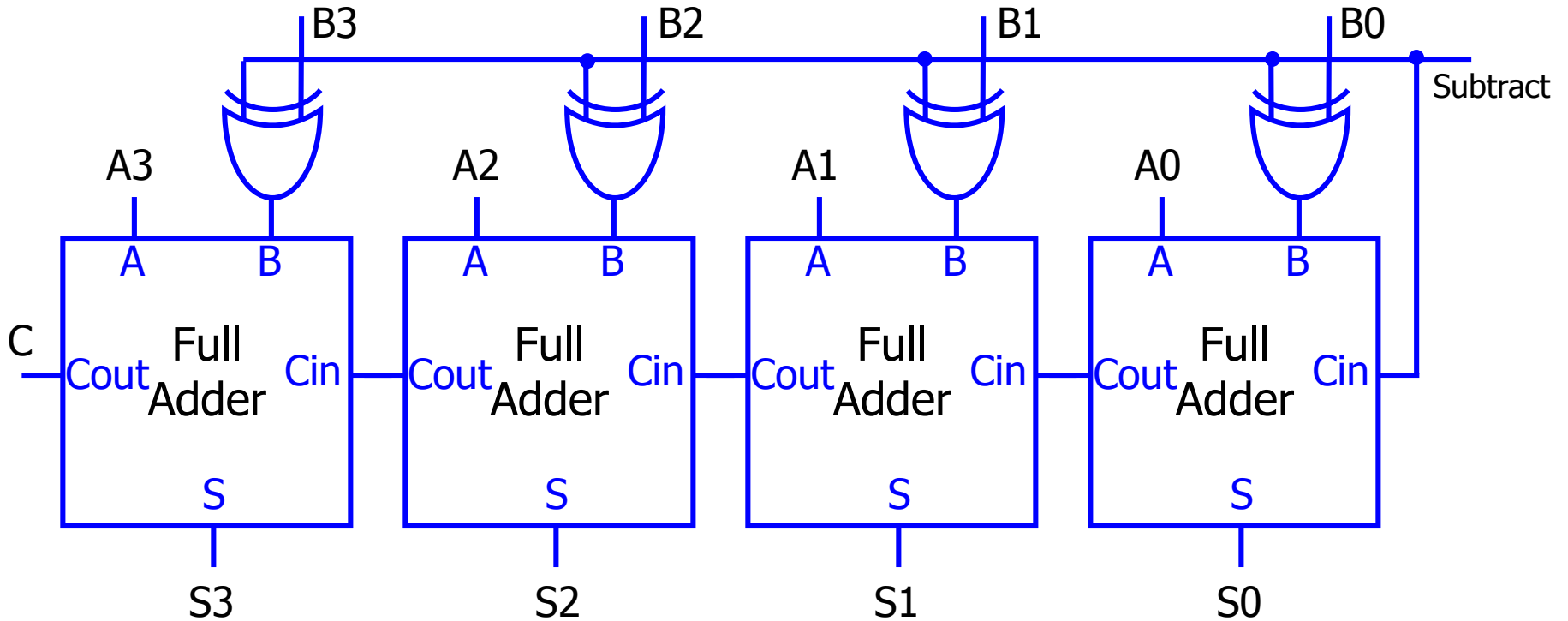

- **$A - B = A + (-B)$** 
  - Take 2's complement of B
  - Perform addition of A and 2's complement of B